
- 1. A current of 240 mA flows in a wire for five minutes. Calculate the a given point in that time.
- 2. When sodium chloride is dissolved in wat an sociates into sodium chloride sociates into sociate sociates into sociate sociates into sociate sociates into socia
- 3. Di Gave her a piece of copper wire would be expected to behave schooratory.
- 4. (a) A 1.50 m long piece of nichrome wire has a resistivity of 1.10 of 5.62 Ω . Calculate the diameter of this wire.
 - (b) A student carried out an investigation to find the resistivity of material. The results are shown in the table.

length of wire / m	mean resistanc
0.10	0.44
0.20	0.81
0.30	1.35
0.40	1.83
0.50,	2.22
9. 0	2.64
<i>)</i> ≥ 0.70	3.02
0.80	3.55

Plot a graph of these results and draw a straight line of best horizontal axis.

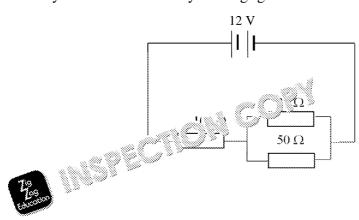- (ii) The wire had a cross-sectional area of 4.7×10^{-7} m². Use graph to determine the resistivity of this wire.
- 5. The diagram to the right shows a circuit containing three resistors. the battery. Assume the battery has negligible internal resistance.




COPYRIGHT PROTECTED




Test 3.3a – Electrons Page 1 of 2

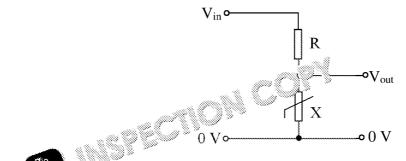6. The circuit diagram below shows part of a sensor in a house. $V_{\rm in}$ is At a particular temperature the ratio of R : X is 3 : 8.



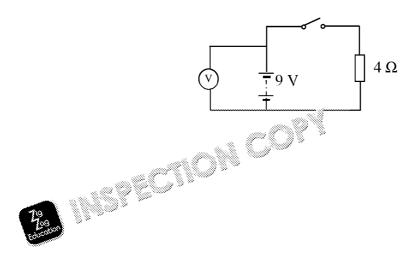- (a) late V_{out} when the ratio of R: X is 3:8.
- (b) Explain what happens to this ratio as the temperature decreases
- 7. The circuit below can be used to determine the internal resistance of circuit has an e.m.f. of 9 V. When the switch is closed, the voltmet Calculate the internal resistance of the battery.





COPYRIGHT PROTECTED



Test 3.3a – Electrons Page 2 of 2

Preview of Questions Ends Here	
Preview of Questions Ends Here This is a limited inspection copy. Sample of questions ends here to avoid students pre questions before they are set. See contents page for details of the rest of the resonance.	
This is a limited inspection copy. Sample of questions ends here to avoid students pre	
This is a limited inspection copy. Sample of questions ends here to avoid students pre	