- 1. A current of $56 \mu A$ flows in a wire for two minutes. Calculate the given point in that time.
- 2. In pure water, fewer than 1 in 5 000 000 color water as ions. To molecules. Explain why pure water the deliberation as an insulator
- 3. Discuss the prece of copper wire would be expected to behave in aquid helium. Liquid helium has a temperature of 4 K
- (a) A 1.65 m long piece of constantan wire has a resistivity of 4.
 of 1.20 Ω. Calculate the diameter of this wire.
 - (b) A student carried out an investigation to find the resistivity of material. The results are shown in the table.


length of wire / m	mean resistanc
0.20	0.56
0.40	1.30
0.60	1.81
0.80	2.54
1.00	3.18
1 %	3.68
1.40	4.21
1.60	4.92



illot a graph of these results and draw a straight line of behorizontal axis.

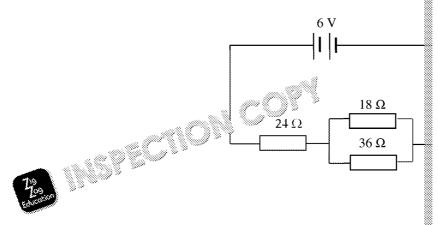- (ii) The wire had a cross-sectional area of 2.1×10^{-7} m². Us graph to determine the resistivity of this wire.
- 5. The diagram shows a circuit containing three resistors.


 Calculate the current through the battery. Assume the battery has



COPYRIGHT PROTECTED



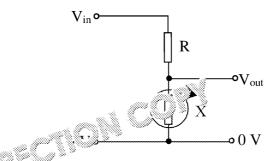
6. The circuit diagram shows part of a sensor in a house.



 V_{ir} 120 V. At a particular light intensity the ratio of R (a) late V_{out} when the ratio of R : X is 1 : 3.

(b) Explain what happens to this ratio as the light intensity decreas

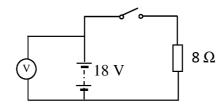7. The circuit below can be used to determine the internal resistance of



The battery in the circuit has an e.m.f. of 18 V. When the switch is closed, the voltmeter read V. Calculate the internal resistance of the pater.





COPYRIGHT PROTECTED



Preview of Questions Ends Here	
Preview of Questions Ends Here This is a limited inspection copy. Sample of questions ends here to avoid students pre questions before they are set. See contents page for details of the rest of the resonance.	
This is a limited inspection copy. Sample of questions ends here to avoid students pre	
This is a limited inspection copy. Sample of questions ends here to avoid students pre	